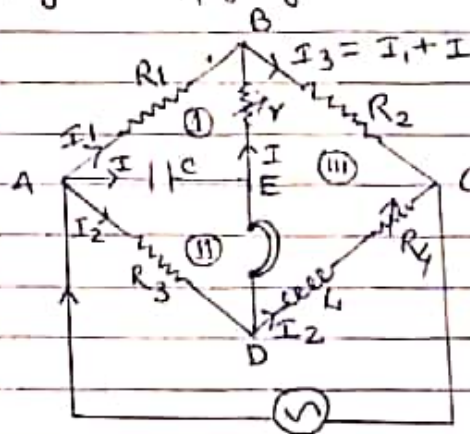


Anderson Bridge D-2 (H & S)
Paper-IV

This is the modified form of Maxwell's L/C bridge. The double balance is obtained by ~~also~~ adjusting resistances only, the standard condenser being invariable. Anderson's bridge shown in fig is formed by placing the condenser C and a non inductive resistance r in series with the condenser, the combination being parallel with R_1 ; the other components and detector are placed as shown in fig. At the time of balance E and D are at the same potential and let the current vectors in the different parts of the bridge be as indicated in fig. Applying Kirchoff's law we have



$$R_1 I_1 - \left(r + \frac{1}{j\omega C} \right) I = 0 \quad [\text{for Loop I}] \quad \text{--- (1)}$$

$$\frac{1}{j\omega C} \cdot I - R_3 I_2 = 0 \quad [\text{for Loop II}] \quad \text{--- (2)}$$

$$R_2 (I_1 + I) + rI - (j\omega L + R_4) I_2 = 0 \quad [\text{for Loop III}] \quad \text{--- (3)}$$

Substituting the value of I_1 & I_2 from equⁿ (1) & (2) in equⁿ (3) we have,

$$\frac{R_2}{R_1} \left(r + \frac{1}{j\omega C} \right) I + R_2 I - \frac{(j\omega L + R_4) I + rI}{j\omega C R_3} = 0 \quad \text{--- (4)}$$

Equating real & imaginary parts, we have

$$\frac{R_2}{R_1} r + R_2 - \frac{L}{CR_3} + r = 0$$

$$\text{or } L = CR_3 \left[\frac{R_2}{R_1} r + R_2 + r \right]$$

$$= CR_3 \left[r \left(1 + \frac{R_2}{R_1} \right) + R_2 \right] \quad \text{--- (5)}$$

$$\text{and } \frac{R_2}{R_1 \omega C} - \frac{R_4}{R_3 \omega C} = 0 \text{ or } \frac{R_1}{R_2} = \frac{R_3}{R_4} \quad \text{--- (6)} \quad \underline{2}$$


These conditions are independent of the frequency of the source and can be satisfied independently of each other by adjusting R_4 in the latter case and r in the former case. Equn (5) shows that balance is possible only when $L > CR_2 R_3$ otherwise r will be negligible negative. Since there is no other inductance all mutual reactions between neighbouring inductance is avoided.

It is best to use $R_1 : R_2 = 1 : 1$

The formula then reduces to

$$R_3 = R_4 \text{ and } L = CR_3(2r + R_2) \quad \text{--- (7)}$$

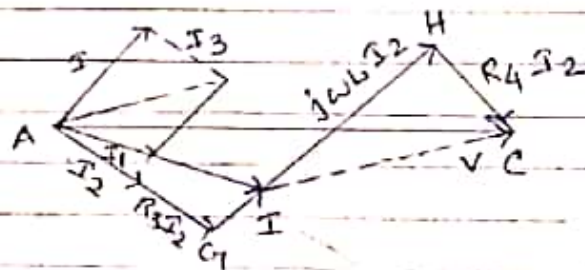The vector diagram for the Anderson bridge is shown below. If \vec{V} is \vec{AC} is \vec{V} , the potential vector for the applied voltage. If I_2 represents the current in ADC, then $AG = R_3 I_2$ and $GH = j\omega L I_2$ and $HC = R_4 I_2$, so that $HC \parallel$ to AG and



$GH \perp$ to AC or HC . Since the potential of F is the same as that of D , hence

$$V_{FE} = V_{AD}$$

$$\text{or } \left(\frac{1}{j\omega C}\right) I = R_3 I_2$$

This relation shows that I is in quadrature with I_2 . If we draw $GI = R I$ then the vector AI is $R_1 I_1$. The vector IC is $R_2 I_3 = R_2 (I_1 + I)$.

First of all the circuit is arranged as simple Wheatstone Bridge connecting the inductance in the 4th arm CD. The resistance R_1 and R_2 are fixed to 10 ohm each and R_3 is varied until the galvanometer deflection changes direction. The expected value is calculated with the formula (6). The expt. is

repeated with $\frac{R_1}{R_2} = 10$ and 100 and the actual resistance in the inductance arm R_2 is calculated. Now R_1 and R_2 are readjusted to the ratio $10:10$ and a fractional resistance R' is placed in series with the inductance. Now R_3 and R_4 , R' are varied for no deflection in the galvanometer. In this case $R_1 + R' = R_4 = R_3$. To increase the sensitivity the resistances are so arranged that $R_1 = R_2 = \frac{1}{2} R_3$.

Now galvanometer and D.C. source are replaced by Headphone and A.C. source respectively and capacitance C and resistance r are inserted as shown in fig. R_1, R_2, R_3 and R_4 are kept as such and the bridge is balanced for minimum sound with the help of resistance r . The expt. may be repeated by taking different capacitances. Substituting these values in eqn (7) self inductance of a given coil can be calculated.