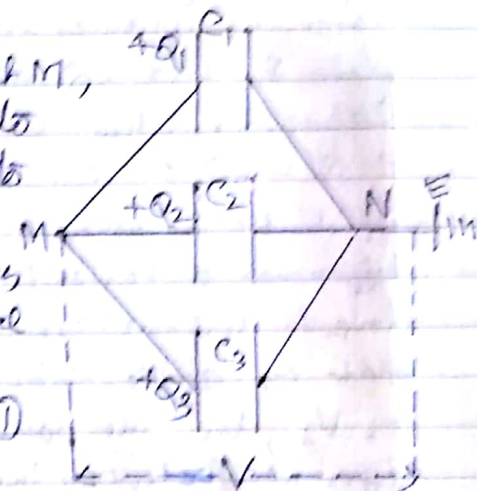


Combination of Capacitors, [contd.---]

(b) In Parallel. In this arrangement, the insulated plates are joined to a common terminal M which is connected with the source of potential, and, similarly, the other plates are joined to another common terminal N which is earthed. It is clear that all the capacitors, being directly connected to the source and the earth, have the same potential difference V .

When a charge is given at M, the charge is distributed to the capacitors according to their capacitances. If Q_1, Q_2, Q_3 be the charges of the capacitors, the total charge



$$Q = Q_1 + Q_2 + Q_3 \dots (1)$$

If C_1, C_2, C_3 be the individual capacitances and C the combined capacitance, we have

$$Q = VC, \quad Q_1 = Q \cdot \frac{C_1}{C}, \quad Q_2 = Q \cdot \frac{C_2}{C}, \quad Q_3 = Q \cdot \frac{C_3}{C} \text{ etc.}$$

Hence from eqn (1)

$$VC = VC_1 + VC_2 + VC_3 \\ = V(C_1 + C_2 + C_3)$$

$$\text{i.e. } C = C_1 + C_2 + C_3 + \dots \quad (2)$$

Thus the combined capacitance of a number of capacitors in parallel is the sum of the separate capacitances.

This arrangement is used when a large capacitance is required to build up out of a number of small capacitance units available.