

A.C Circuit : Reactance

An inductance offers no resistance in a steady current but when the current is varying as in a.c circuit, a back e.m.f is set up in the inductance. This reduces the current and thus is equivalent to a resistance.


The resistance due to inductance in an a.c circuit is called its reactance and is expressed in ohms. It is denoted by X_L .

$$\text{Reactance} = \omega L = 2\pi fL$$

Thus reactance is not a const. quantity but is directly proportional to the freq. of the applied e.m.f.

vector diagram:- The voltage across the resistance is in phase with the current through it, the voltage across the inductance leads the current in phase by 90° . We thus may represent these voltages by vectors. The P.D across the resistance is represented by the vector $\vec{OA}$. The vector $\vec{AB}$ represents the magnitude and direction of the P.D across the inductance and is drawn 90° to the vector $\vec{OA}$.

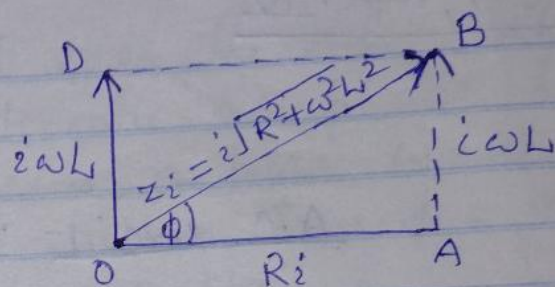The resultant vector OB will represent the combined P.D across the inductance and resistance in series,



$$\vec{OB} = \vec{OA} + \vec{AB}$$

$$OB = \sqrt{OA^2 + AB^2}$$

$$\text{or } Z = \sqrt{R^2 + \omega^2 L^2}$$

$$\text{and } \tan \phi = \frac{\omega L}{R}$$

By the use of operator j : In cartesian co-ordinates a unit vector is taken along the +ve x-axis. The multiplication by the imaginary quantity j denotes the rotation of the positive unit vector counter clock wise through 90° . Thus j is along the y-axis. Thus

$$e = Ri + j\omega Li$$

$$\therefore i = \frac{e}{R + j\omega L} = \frac{e}{Z}$$

where $Z = R + j\omega L$ is known as complex impedance. The real part is called the resistance resistive or inphase component and the imaginary part as the reactive or quadrature component.

$$Z = R + j\omega L = Z e^{j\phi} = Z(\cos \phi + j \sin \phi)$$

$$\therefore Z = \sqrt{R^2 + \omega^2 L^2} \text{ and } \tan \phi = \omega L / R$$

